



A blank worksheet template for a 3rd-grade math activity. The page is divided into several sections:

- Title Box:** A large rectangular box at the top center for the student's name or title.
- Equation Lines:** A series of horizontal lines across the middle of the page, separated by a vertical line, for writing math equations.
- Answer Grid:** A grid of six small squares on the right side, arranged in two rows of three, for writing the answers to the equations.

A schematic diagram of a parallel circuit. At the top, a battery is represented by a long horizontal line connected to a rectangular box. Below the battery, the circuit splits into six parallel branches, each containing a light bulb represented by a circle with a filament. The branches rejoin at the bottom, which is connected back to the battery.

[illegible][illegible]